


Homework Assignment #6

Due at 11:59 pm, Friday, October 4th, in the BrightSpace Homework 6 dropbox. Submit one and only one PDF file that includes any MatLab code and plot printouts. Start each problem on a new page.

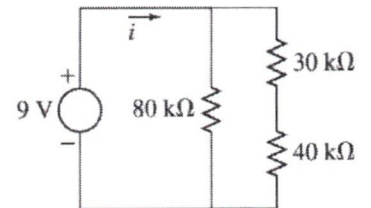
- 1) Determine the equivalent resistance for:

a)

$$R_{eq} = \frac{1}{\frac{1}{80\text{ k}\Omega} + \frac{1}{(30+40)\text{ k}\Omega}} = 37.33\Omega$$




b)

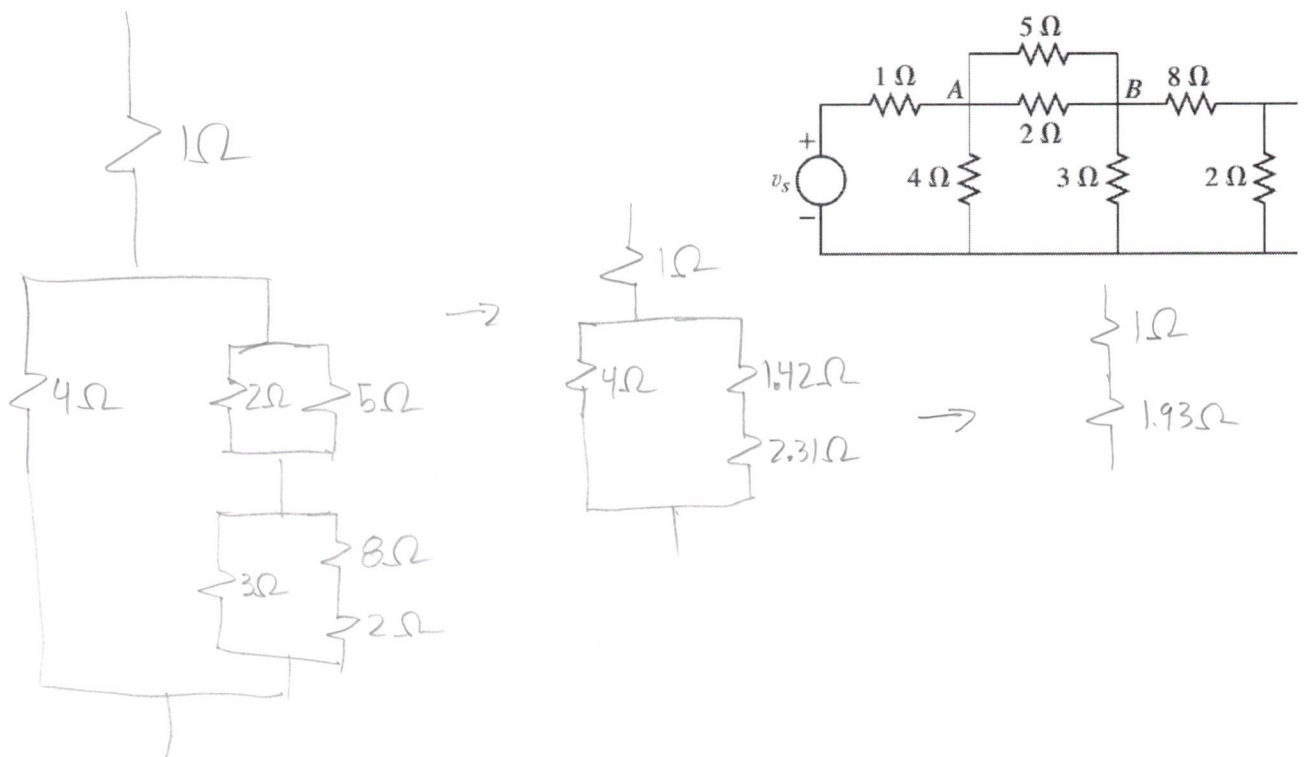

$$R_{eq} = 2.93\Omega$$

Homework Assignment #6

2) For the following circuit:

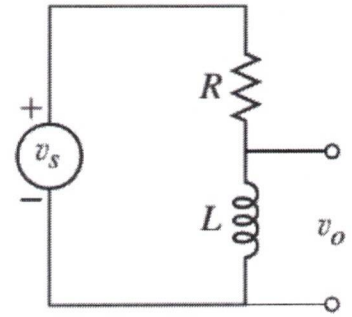

- a) Obtain the model (ODE) of the voltage v_o , given the supply voltage v_s

$$V_s - V_R - V_o = 0$$

$$L = \frac{1}{R} (V_s - V_o)$$

$$\dot{L} = \frac{1}{R} (\dot{V}_s - \dot{V}_o)$$

$$V_o = L \dot{i}$$

$$V_o = \frac{L}{R} (\dot{V}_s - \dot{V}_o)$$

$$\frac{L}{R} \dot{V}_o + V_o = \frac{L}{R} \dot{V}_s$$

$$\dot{V}_o + \frac{R}{L} V_o = \dot{V}_s$$

- b) Determine the transfer function: $\frac{V_o(s)}{V_s(s)} = \frac{s}{s + \frac{R}{L}} = \frac{Ls}{Ls + R}$

- c) Use the Laplace Transform method to determine $v_o(t)$

if: $v_s = 7.5u(t)$, $R = 8 \Omega$ and $L = 5.3 \times 10^{-3} \text{ H}$.

Use Matlab to plot your solution equation.


$$V_o = \frac{Ls}{Ls + R} \left(\frac{A}{s} \right) = \frac{AL}{Ls + R} = \frac{A}{s + R/L}$$

$$v_o(t) = A e^{-\frac{R}{L}t}$$

- d) Use the your transfer function from part b), and Matlab tf() and step() functions to plot the response $v_o(t)$, and compare to part c).

Homework Assignment #6

3) For the following circuit:

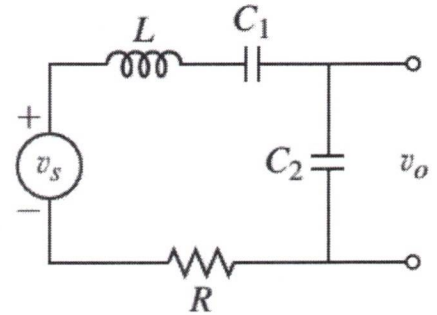

- a) Obtain the model (ODE) of the voltage v_o , given the supply voltage v_s

$$V_s - V_L - V_{C_1} - V_o - V_R = 0$$

$$V_s - L\dot{i} - \frac{1}{C_1} \int i dt - V_o - iR = 0$$

$$\dot{V}_s - L\ddot{q} - \frac{1}{C_1} i - \dot{V}_o - iR = 0$$

$$LC_2 \ddot{V}_o + RC_2 \dot{V}_o + \left(1 + \frac{C_1}{C_2}\right) \dot{V}_o = \dot{V}_s$$

$$LC_2 \ddot{V}_o + RC_2 \dot{V}_o + \left(1 + \frac{C_1}{C_2}\right) V_o = V_s$$

$$V_o = \frac{1}{C_2} \int i dt$$

$$\dot{V}_o = \frac{1}{C_2} i$$

$$\ddot{V}_o = \frac{1}{C_2} \dot{i}$$

$$\ddot{V}_o = \frac{1}{C_2} \ddot{q}$$

- b) Determine the transfer function:

$$\frac{V_o(s)}{V_s(s)} = \frac{1}{LC_2 s^2 + RC_2 s + \left(1 + \frac{C_1}{C_2}\right)}$$

- c) Use the Laplace Transform method to determine $v_o(t)$

for: $v_s = 3u(t)$, $R = 4 \Omega$, $L = 6 \times 10^{-3} \text{ H}$ and $C_1 = C_2 = 6.5 \times 10^{-4} \text{ N} \cdot \text{m} \cdot \text{s/rad}$

Then, use Matlab to plot your solution equation.

$$V_o = \frac{A}{s} \left(\frac{1}{LC_2 s^2 + RC_2 s + \left(1 + \frac{C_1}{C_2}\right)} \right) = \frac{A}{LC_2 s} \left(\frac{1}{s^2 + \frac{R}{L} s + \frac{(1 + C_1/C_2)}{LC_2}} \right)$$

$$V_o = \frac{A}{\left(1 + \frac{C_1}{C_2}\right)} \left(\frac{\frac{(1 + C_1/C_2)}{LC_2}}{s \left(s^2 + \frac{R}{L} s + \frac{(1 + C_1/C_2)}{LC_2} \right)} \right)$$

$$V_o(t) = \frac{A}{\left(1 + \frac{C_1}{C_2}\right)} \left[1 - \frac{1}{\sqrt{1 - \zeta^2}} e^{-\zeta \omega_n t} \sin(\omega_n \sqrt{1 - \zeta^2} t + \phi) \right]$$

$\omega_n^2 = \frac{(1 + \frac{C_1}{C_2})}{LC_2}$
 $\zeta = \frac{R}{2L\omega_n}$
 $\phi = \arctan\left(\frac{\sqrt{1 - \zeta^2}}{\zeta}\right)$

- d) Use the Matlab ode45() function to plot the response $v_o(t)$, and compare to part c).


Homework Assignment #6

4) Determine the transfer function for the following op-amp circuits:

a)

$$Z_f = \frac{1}{Cs}$$

$$Z_i = R$$

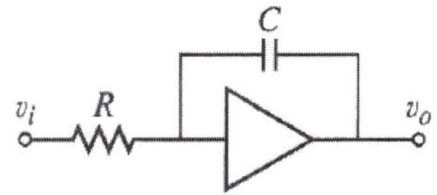


$$\frac{V_o(s)}{V_s(s)} = -\frac{Z_f}{Z_i} = -\frac{1}{RCs}$$

b)

$$Z_f = \frac{1}{\frac{1}{R_4} + \frac{1}{R_3 + C_2 s}}$$
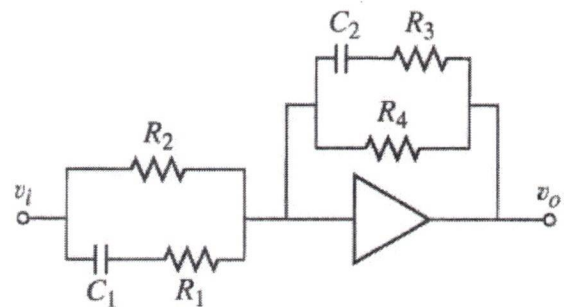
$$Z_i = \frac{1}{\frac{1}{R_2} + \frac{1}{R_1 + C_1 s}}$$




$$\frac{V_o(s)}{V_s(s)} = -\frac{Z_f}{Z_i} = -\frac{\frac{1}{R_2} + \frac{1}{R_1 + C_1 s}}{\frac{1}{R_4} + \frac{1}{R_3 + C_2 s}}$$

```
1 clear all
2 clc
3 clf
4
5 %% Problem 2
6
7 A = 7.5;    R = 8;    L = 5.3e-3;
8
9 num = [L,0];
10 den = [L, R];
11 T = tf(num,den);
12 [vo_sim, t1] = step(T);
13
14 vo = A * exp(-R/L .* t1);
15
16 figure(1)
17 title('Simulation')
18 plot(t1,A*vo_sim)
19 xlabel('Time - [s]')
20 ylabel('Voltage - [V]')
21
22 figure(2)
23 title('Analytic Solution')
24 plot(t1,vo)
25 xlabel('Time - [s]')
26 ylabel('Voltage -[V]')
27
28 figure(3)
29 title('Comparison')
30 plot(t1,A*vo_sim,t1,vo)
31 xlabel('Time - [s]')
32 ylabel('Voltage -[V]')
33 legend('Simulation','Analytical')
34
35 %% Problem 3
36 global R;
37 global L;
38 global C1;
39 global C2;
40 global A;
41
42 R = 4; L = 6e-3; C1 = 6.5e-4; C2 = 6.5e-4; A = 3;
43
44 [t2,states] = ode45(@deriv,[0,0.1],[0,0]);
45
46 wn = sqrt(((1 + C1/C2))/(L*C2));
47 z = (R/L)/(2*wn);
48 sz = sqrt(1-z^2);
49 phi = atan(sz/z);
50 ex = -z.*wn.*t2;
51
52 C1 = A/(1 + C1/C2);
53
54 v1 = C1.*(1-(exp(ex).*sin(wn.*sz.*t2+phi))/sz) ;
55
56 figure(4)
57 plot(t2,states(:,1))
58 title('Simulation')
59 xlabel('Time - [s]')
60 ylabel('Voltage - [V]')
```


```
61
62 figure(5)
63 plot(t2,v1)
64 title('Analytical')
65 xlabel('Time - [s]')
66 ylabel('Voltage - [V]')
67
68 figure(6)
69 plot(t2,states(:,1),t2,v1)
70 title('Comparison')
71 xlabel('Time - [s]')
72 ylabel('Voltage - [V]')
73 legend('Simulation','Analytical')
74
75 function XDOT = deriv(t,X)
76     % System Parameters
77     global R;
78     global L;
79     global C1;
80     global C2;
81     global A;
82
83     % Rename states
84     vo = X(1); vod = X(2);
85
86     % Initiate forcing function
87     vs = A;
88     % write the non-trivial equations using nice names
89     vodd = (vs - R*C2*vod - (1 + C1/C2)*vo)/(L*C2);
90
91     XDOT = [ vod; vodd] ; %return the derivative values
92 end
```

Problem 2

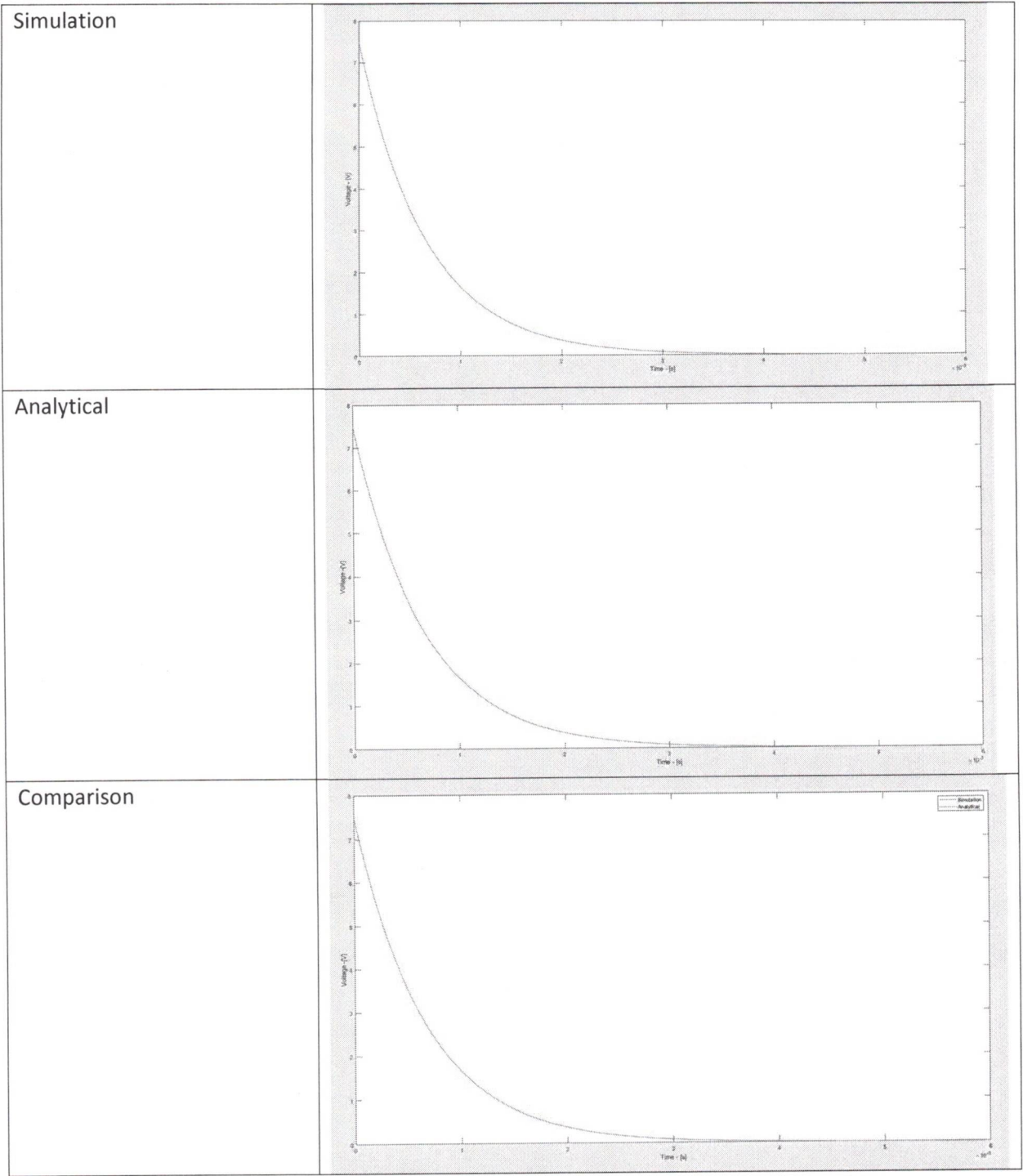


Problem 3

Simulations

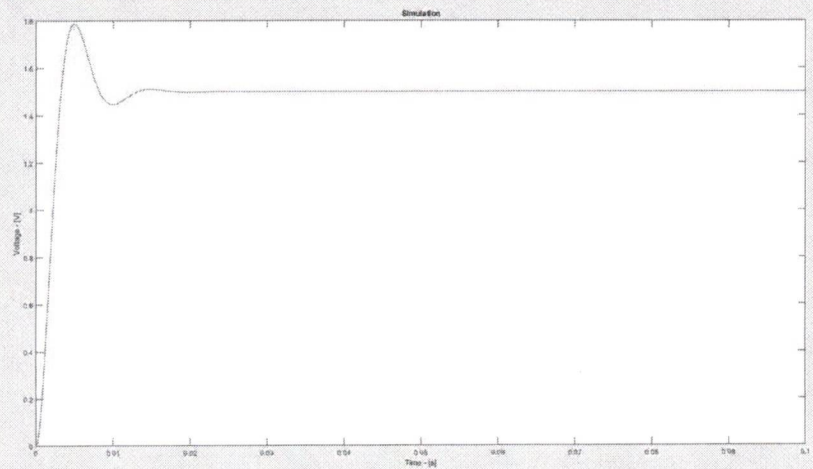

Analytical

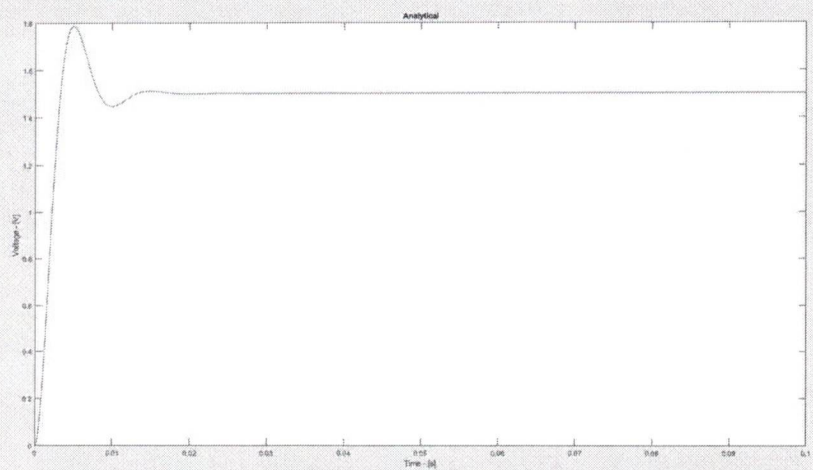

Comparison

